



**AIR UNIVERSITY**  
**DEPARTMENT OF MECHATRONICS ENGINEERING**

**H-BRIDGE CIRCUIT**

**GROUP MEMBERS**

221658 – EDEN JOSEPH

221748 – MUHAMMAD ABDULLAH KHAN

221751 – EHAB KHAN

**SUBMITTED TO**

Engr. Umer Farooq And Engr. Muzzamil Ghaffar

**SPRING 2023**

## ABSTACT

---

**T**HIS semester project is related to dc motor and directional control. An H-Bridge will allow us to control direction of motors in RC Cars or other machines. In the future we can try to reduce its size as much as we can and use our own H-Bridges in Our RC Cars etc. As its applications are already discussed above so, we have a lot of idea about it.

Our project is in working condition and gave a lot of experience and got us better at stuff.

# CONTENTS

---

## **1 Introduction**

- 1.1 Definition
- 1.2 Starting Information
- 1.3 Design Plan

## **2 Simulations And Components**

- 2.1 Initial Design
- 2.2 Schematic
- 2.3 PCB layout
- 2.4 Simulation
- 2.5 Components
- 2.6 Bill Of Materials

## **3 Readings And Measurements**

- 3.1 Power Supplies
- 3.2 Measurements Across Mosfets
- 3.3 Measurements Across Motor

## **4 Practical Implementations**

- 4.1 Breadboard
- 4.2 PCB
- 4.3 Drop Test And Finalization
- 4.4 Bench Test

## **5 Conclusion**

- 5.1 Summary
- 5.2 Conclusion

# 1 INTRODUCTION

---

## 1.1 Definition

“An H-bridge is an electronic circuit that switches the polarity of voltage applied to a load. These circuits are often used in robotics and other applications to allow DC motors to run **forwards** or **backwards**. The name is derived from its common schematic diagram representation, with four switching elements configured as the branches of a letter "H" and the load connected as the cross-bar”

## 1.2 Starting Information

We were asked to design an H bridge circuit to control the direction of a motor with optical isolation and flyback diode, the motor runs at 9V and draws a maximum of 2A current. The motor is to operate continuously for 15 minutes.

We only knew that an H-Bridge is used in RC cars or other motor controlled devices and is used to switch the direction of motor that is clockwise or anti clockwise

## 1.3 Design Plan

We planned to design this circuit using mosfets as it was providing the best voltages and the design was easy execute and we wanted to try something new. Before that I tried to make designs using BJTs but they were not up to the


expectations so I designed it using mosfets and it worked incredibly well so, we proceeded with this design.

## 2 Simulation And Components


---
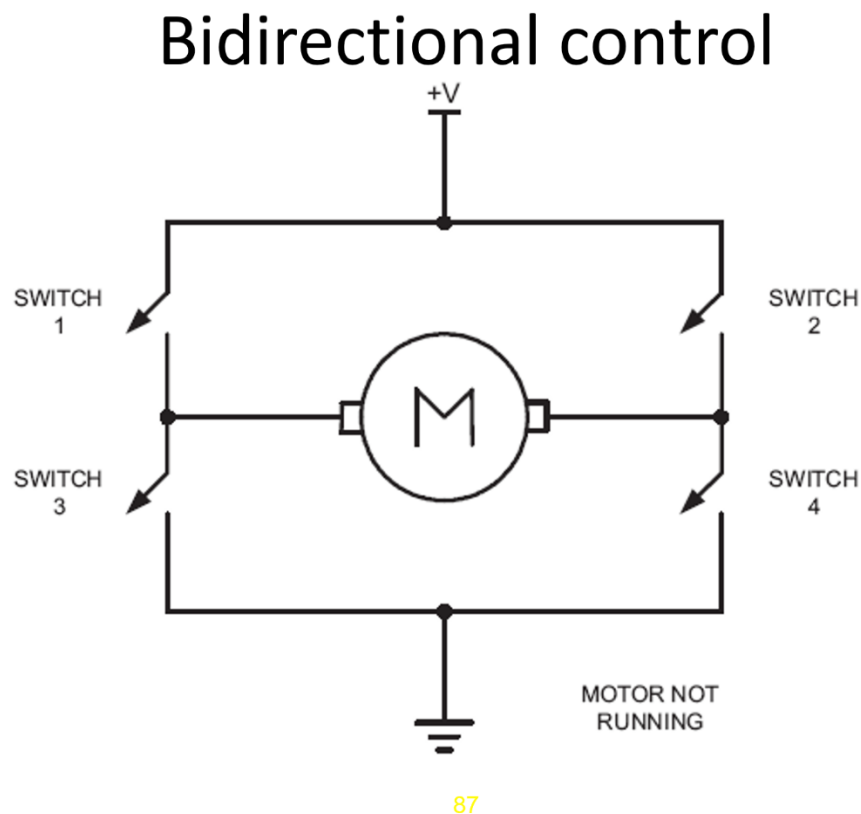
### 2.1 Initial Design

To Start with the Project, we got the initial design provided as following:




## Bidirectional (clock wise)

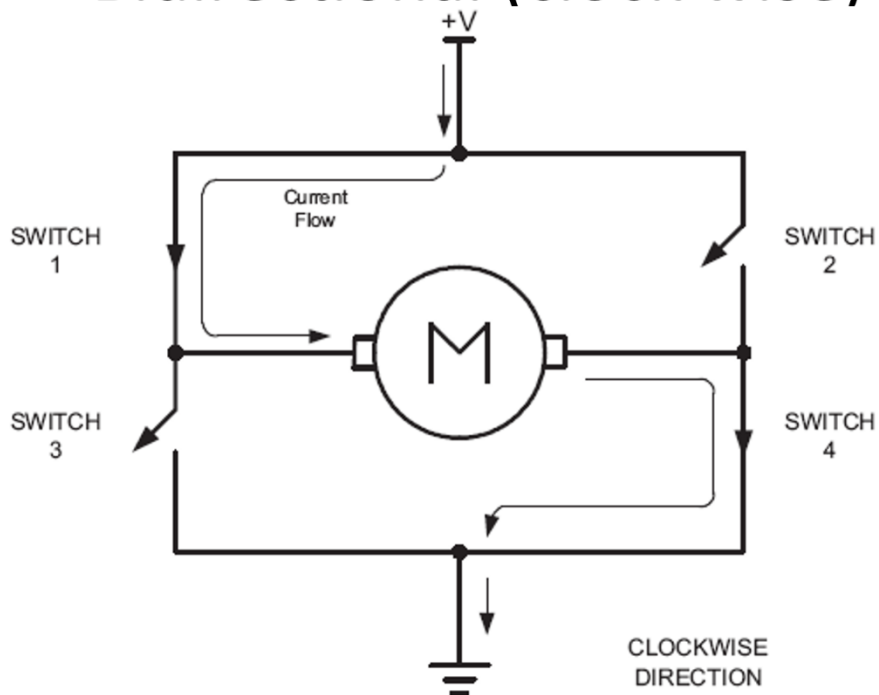


88


## Bidirectional (counter clockwise)

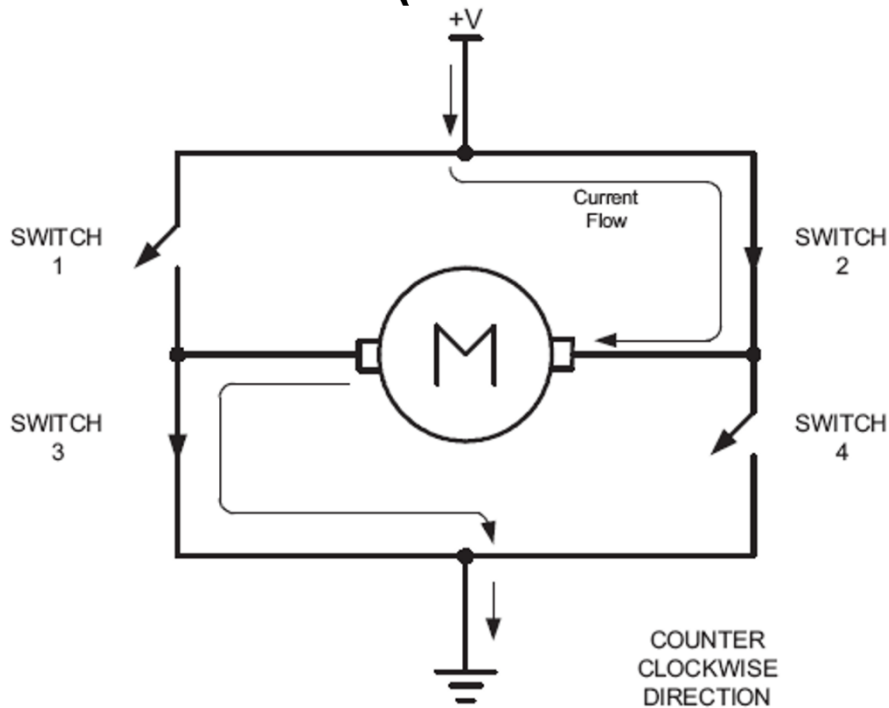


# Bidirectional

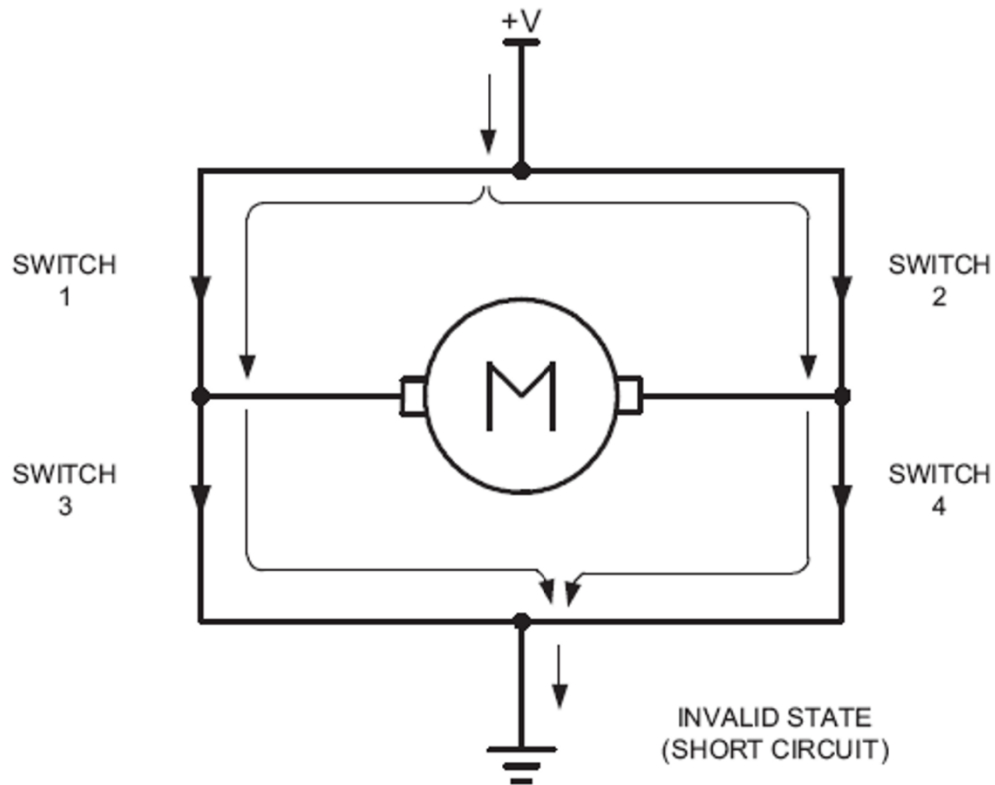


The Initial Schematic Was As Follows:

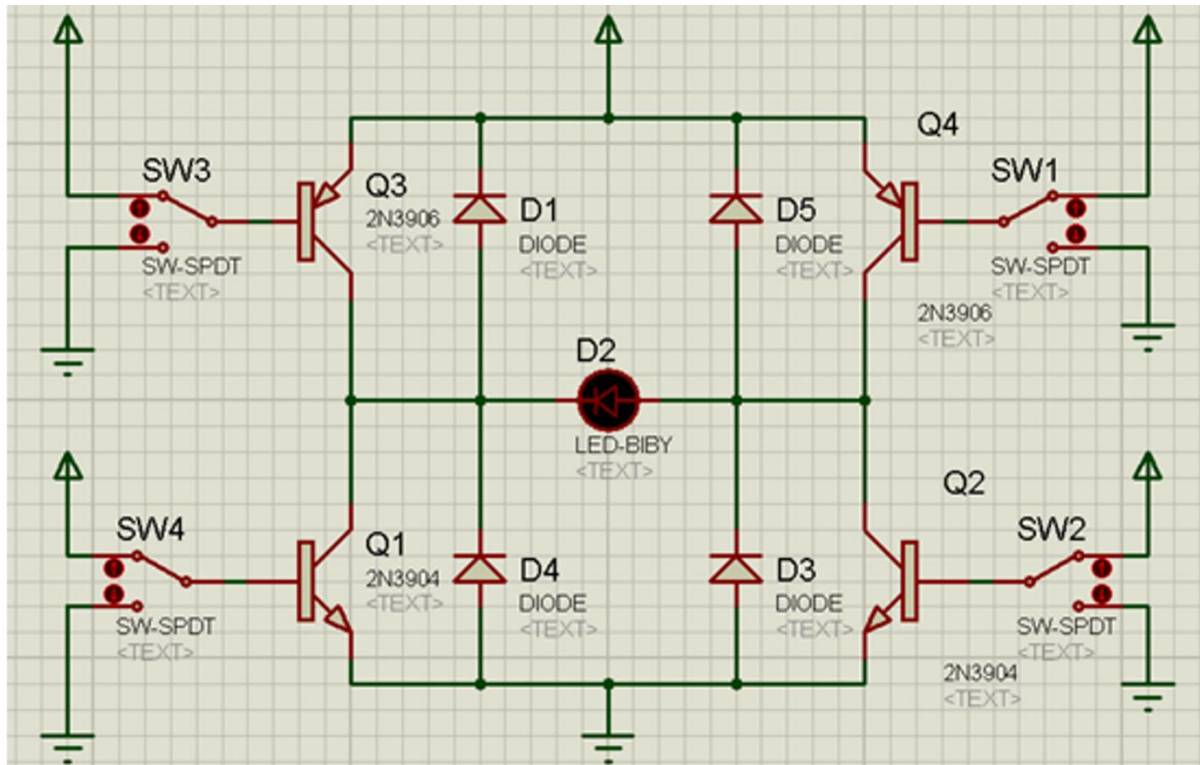

## SEMESTER PROJECT 2 H-BRIDGE CIRCUIT

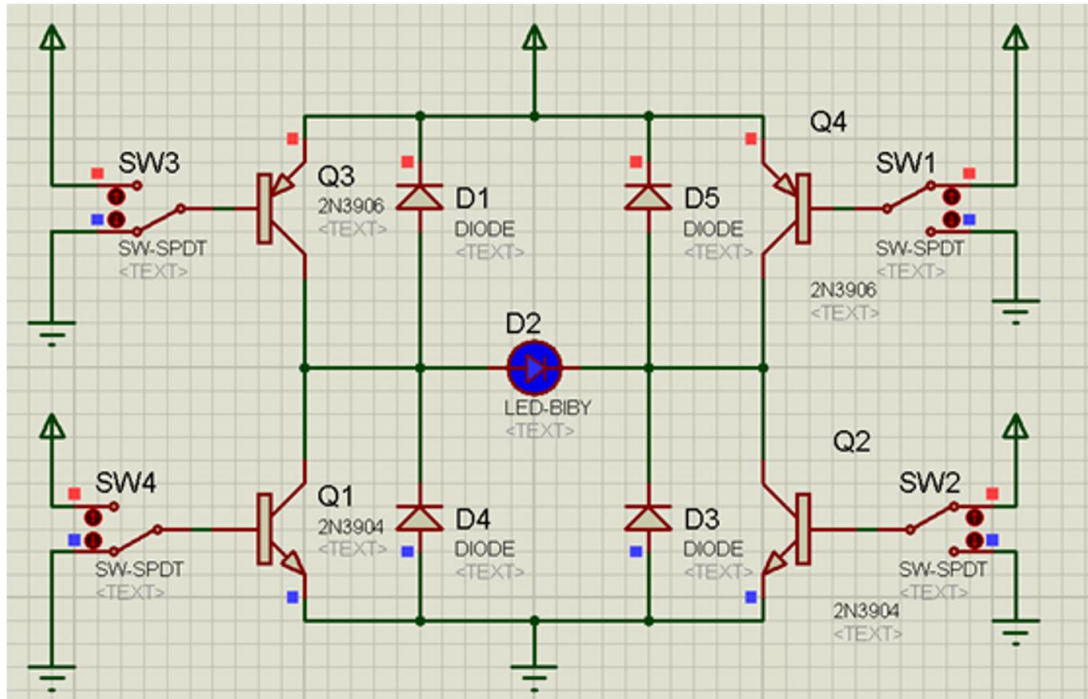

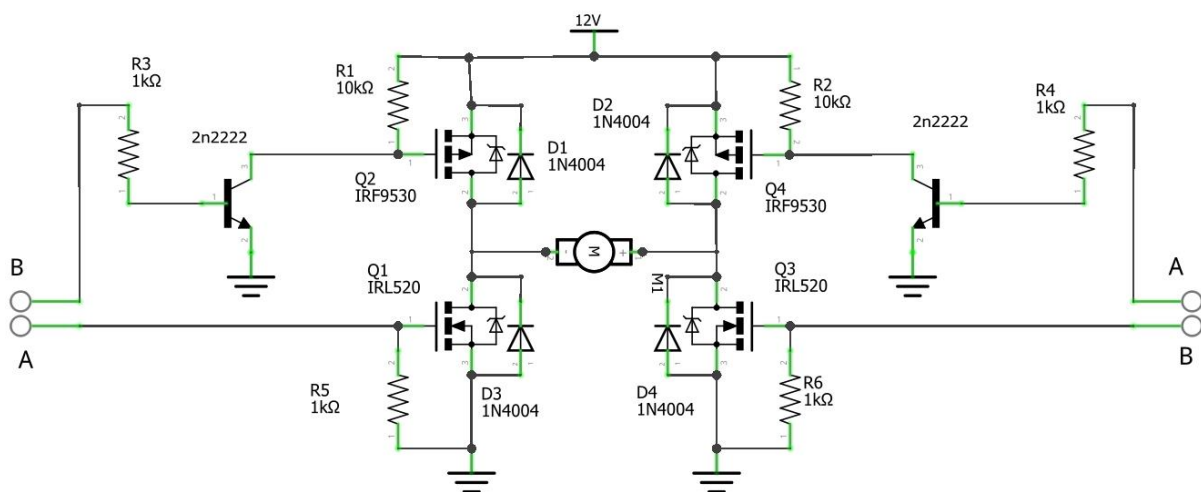
**The Design We Finalized On Paper Is As Following:**





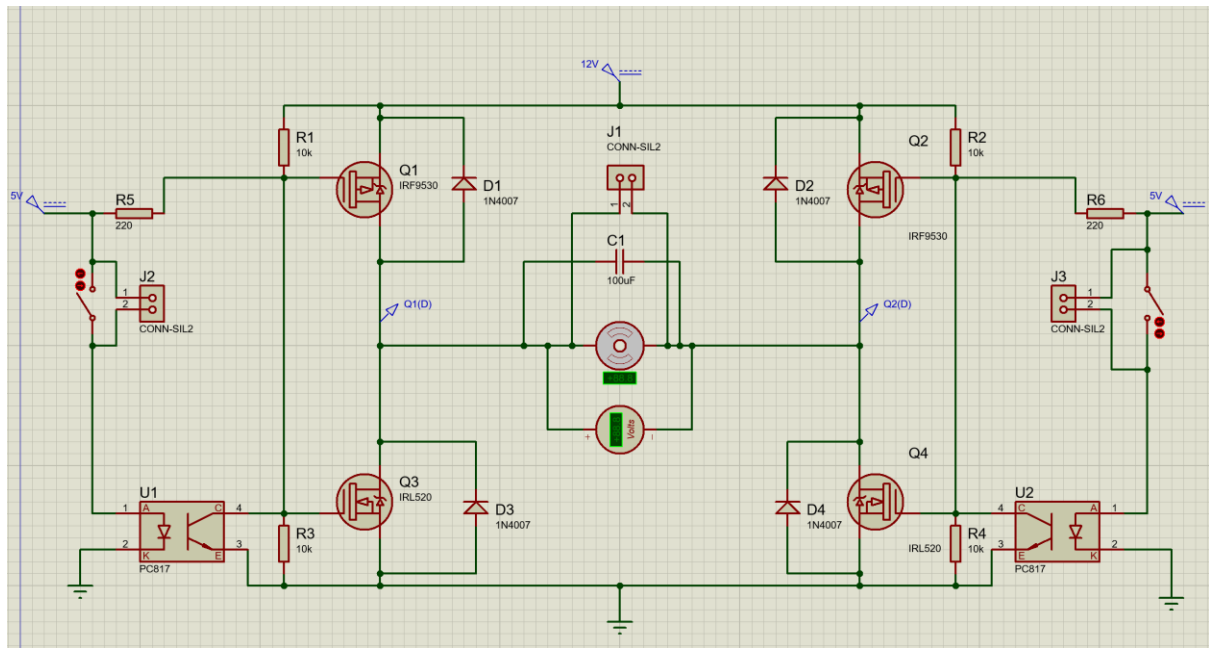
## 2.2 Schematic


The Schematic Layout on Proteus is Designed Like This :



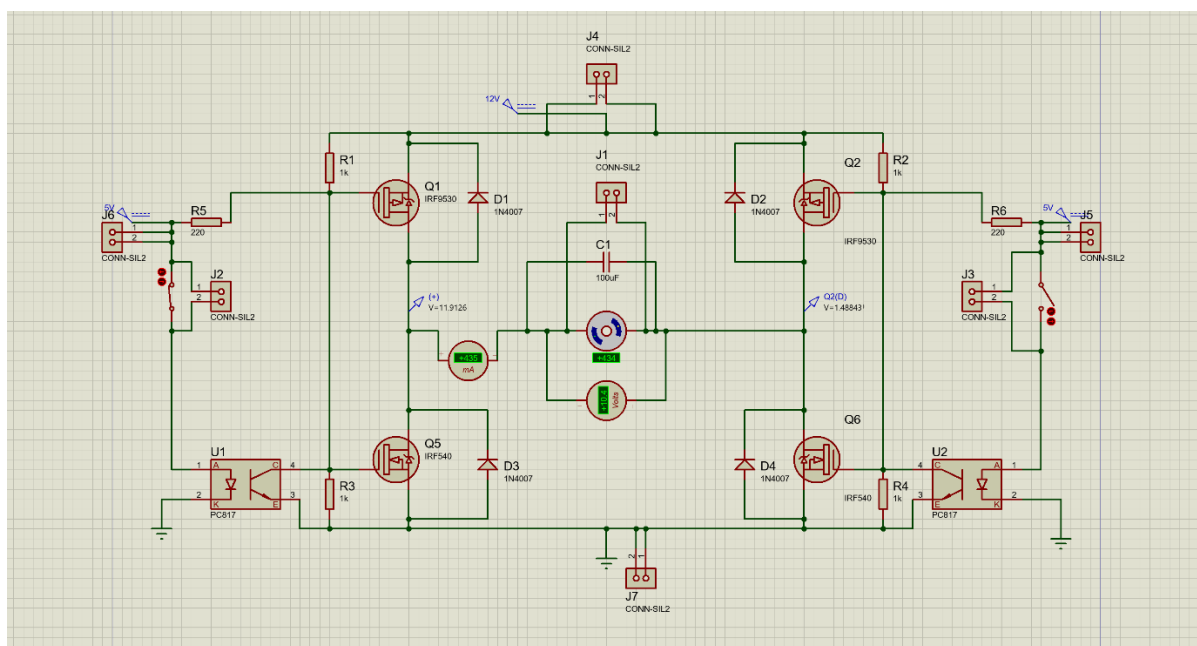
### The Maximum Settings It Can Go On Are:




## 2.3 PCB

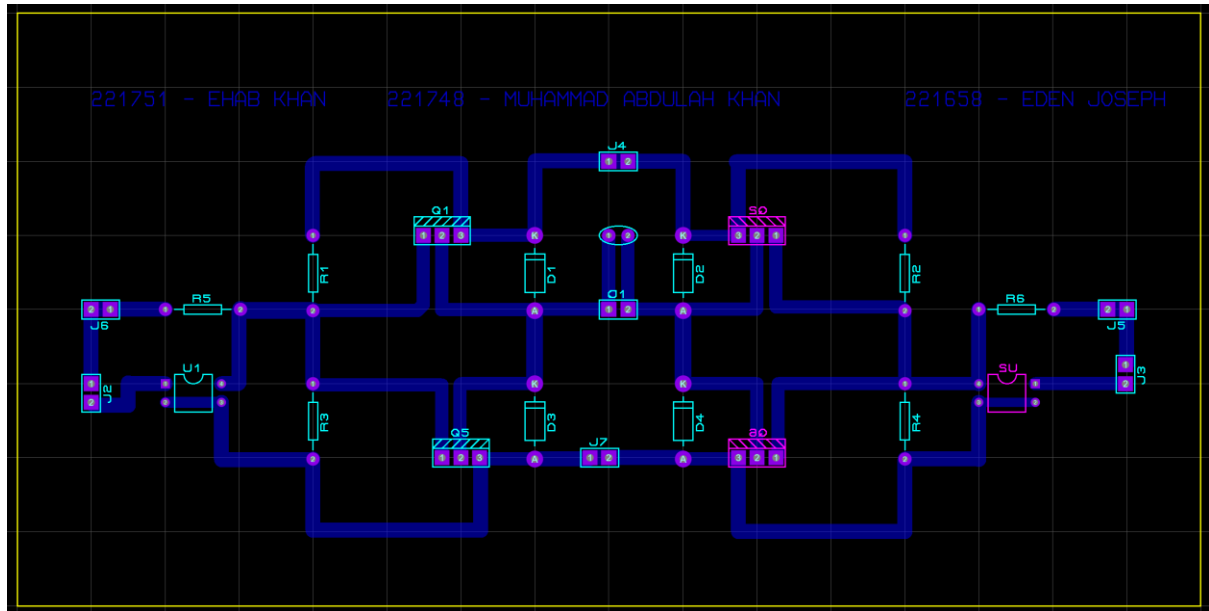

PCB Print Is Provided Below :

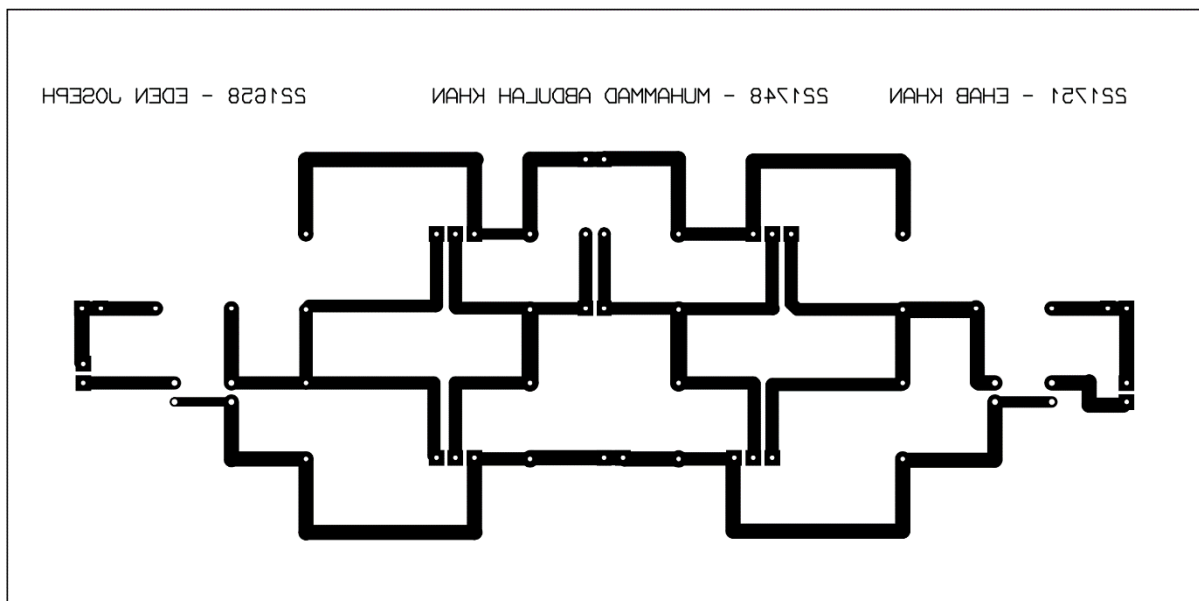

## 2.4 Simulation

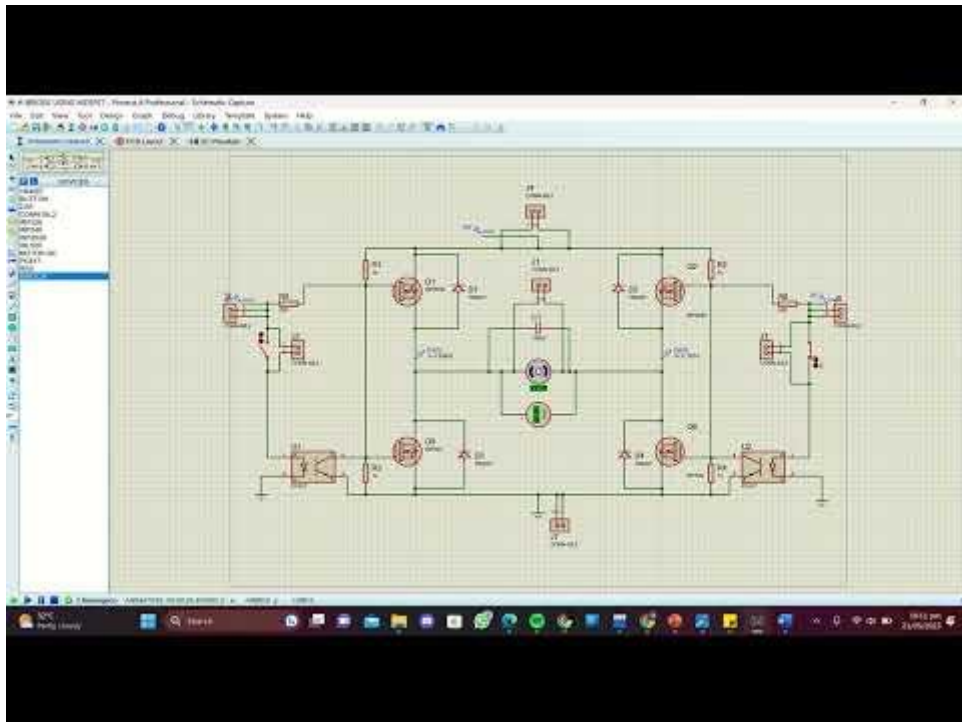

## 2.5 Components

| ITEM      | VALUE                                |
|-----------|--------------------------------------|
| RESISTORS | 1k $\Omega$ AND 470 $\Omega$         |
| CAPACITOR | 100uF                                |
| DC MOTOR  | MAXIMUM 9V                           |
| MOSFETS   | P-TYPE (IRF 9530) , N-TYPE (IRF 540) |

SEMESTER PROJECT 2  
H-BRIDGE CIRCUIT

|             |                           |
|-------------|---------------------------|
| DIODES      | 1N4007                    |
| OPTOCOUPERS | PC817                     |
| CONNECTORS  | 6-PIN SILICONE CONNECTORS |

## 2.6 Bill Of Material

### Bill Of Materials for H-BRIDGE USING MOSFET

**Design Title** H-BRIDGE USING MOSFET  
**Author**  
**Document Number**  
**Revision**  
**Design Created** Wednesday, 10 May 2023  
**Design Last Modified** Wednesday, 10 May 2023  
**Total Parts In Design** 20

#### 0 Modules

| Quantity    | References | Value | Stock Code | Unit Cost |
|-------------|------------|-------|------------|-----------|
| Sub-totals: |            |       |            | Rs0.00    |

#### 1 Capacitors

| Quantity    | References | Value | Stock Code | Unit Cost |
|-------------|------------|-------|------------|-----------|
| 1           | C1         | 100uF |            |           |
| Sub-totals: |            |       |            | Rs0.00    |

#### 6 Resistors

| Quantity    | References | Value | Stock Code | Unit Cost |
|-------------|------------|-------|------------|-----------|
| 4           | R1-R4      | 10k   |            |           |
| 2           | R5-R6      | 220   |            |           |
| Sub-totals: |            |       |            | Rs0.00    |

#### 2 Integrated Circuits

| Quantity    | References | Value | Stock Code | Unit Cost |
|-------------|------------|-------|------------|-----------|
| 2           | U1-U2      | PC817 |            |           |
| Sub-totals: |            |       |            | Rs0.00    |

#### 4 Transistors

| Quantity    | References | Value   | Stock Code | Unit Cost |
|-------------|------------|---------|------------|-----------|
| 2           | Q1-Q2      | IRF9530 |            |           |
| 2           | Q3-Q4      | IRL520  |            |           |
| Sub-totals: |            |         |            | Rs0.00    |

#### 4 Diodes

| Quantity    | References | Value  | Stock Code | Unit Cost |
|-------------|------------|--------|------------|-----------|
| 4           | D1-D4      | 1N4007 |            |           |
| Sub-totals: |            |        |            | Rs0.00    |

#### 3 Miscellaneous

| Quantity    | References | Value     | Stock Code | Unit Cost |
|-------------|------------|-----------|------------|-----------|
| 3           | J1-J3      | CONN-SIL2 |            |           |
| Sub-totals: |            |           |            | Rs0.00    |

|                |  |  |  |               |
|----------------|--|--|--|---------------|
| <b>Totals:</b> |  |  |  | <b>Rs0.00</b> |
|----------------|--|--|--|---------------|

Wednesday, 10 May 2023 6:01:25 pm

SEMESTER PROJECT 2  
H-BRIDGE CIRCUIT

# OCEANA ELECTRONICS

**Deals In: Basic Electronics & Industrial Spare Parts**

G-642, DAV College Road, Rawalpindi. Tel: 5555474  
Fax: 5538108, Email: oceanaelectronics@yahoo.com

Deals in:  
 1. Resistor, Capacitors and Ics.  
 2. All Semi Conductor Devices.  
 3. Industrial Electronics Parts.  
 4. Wireless & Telephone Spare Parts.  
 5. Cables & Wire Used In Electronic Circuits.  
 6. Optonic & SMD Components.

Cash Memo
Date \_\_\_\_\_

Bill No. 8435

Customer Name \_\_\_\_\_

| S.No. | DESCRIPTION  | Qty | Rate         | Amount      |
|-------|--------------|-----|--------------|-------------|
| 1     | P.C.B        |     |              | 300         |
| 2     | Material     |     |              | 250         |
| 3     | P.C. 817     |     |              | 80          |
| 4     | M. S. P.L    |     |              | 400         |
| 5     | R.C.D        |     |              | 50          |
| 6     | male to male |     |              | 250         |
| 7     |              |     |              |             |
| 8     |              |     |              |             |
| 9     |              |     |              |             |
| 10    |              |     |              |             |
| 11    |              |     |              |             |
| 12    |              |     |              |             |
| 13    |              |     |              |             |
| 14    |              |     |              |             |
| 15    |              |     |              |             |
| 16    |              |     |              |             |
| 17    |              |     |              |             |
| 18    |              |     |              |             |
|       |              |     | <b>TOTAL</b> | <b>1330</b> |

Note: Things once sold are not returned or replaced. Signature \_\_\_\_\_

### 3 Readings And Measurements

---

#### 3.1 Power Supply

The voltages at the power supplies are:

12V Main Supply DC  
5V At The Switches

#### 3.2 Measurements Across Mosfets

##### Q1

|   |          |
|---|----------|
| D | 110.4 mV |
| G | 12.00 V  |
| S | 12.00 V  |

##### Q2

|   |          |
|---|----------|
| D | 11.90 V  |
| G | 46.81 mV |
| S | 12.00 V  |

##### Q3

|   |          |
|---|----------|
| D | 110.4 mV |
| G | 4.99 V   |
| S | 0.00 V   |

#### Q4

|   |             |
|---|-------------|
| D | 11.90 V     |
| G | 500 $\mu$ V |
| S | 0.00 V      |

### 3.3 Measurements Across Motor :


|         |        |
|---------|--------|
| VOLTAGE | 10.4 V |
| CURRENT | 435 mA |




## 4 Practical Implementation

---

### 4.1 Breadboard

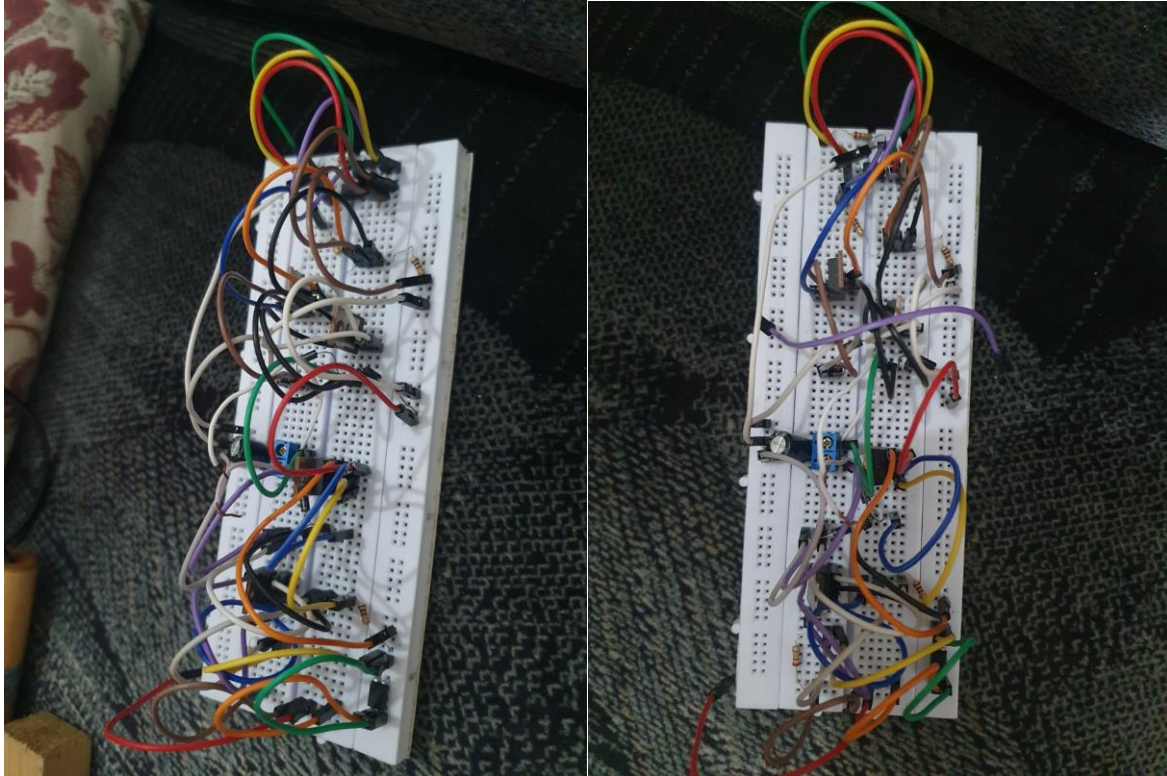


### 4.2 PCB

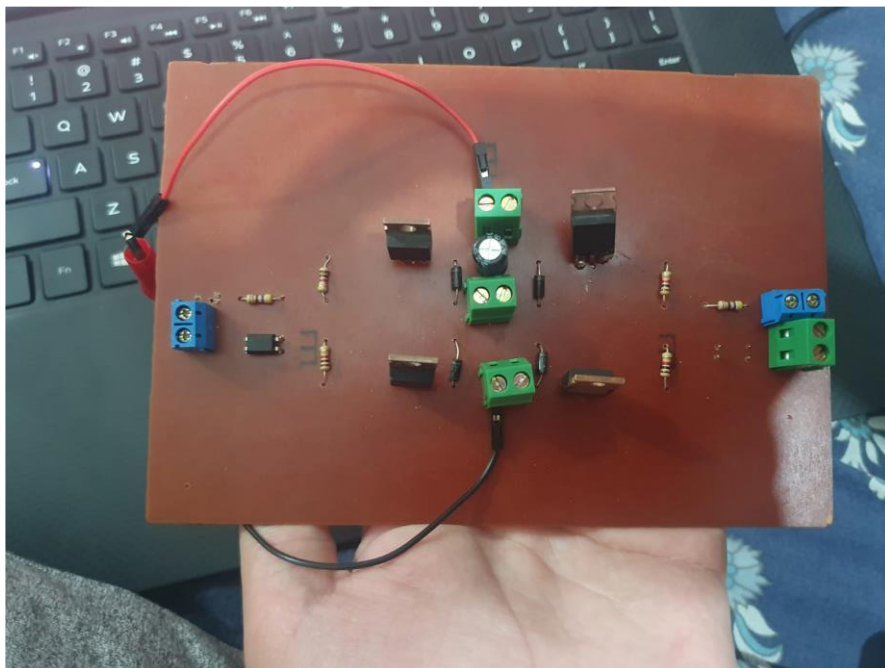




## SEMESTER PROJECT 2 H-BRIDGE CIRCUIT

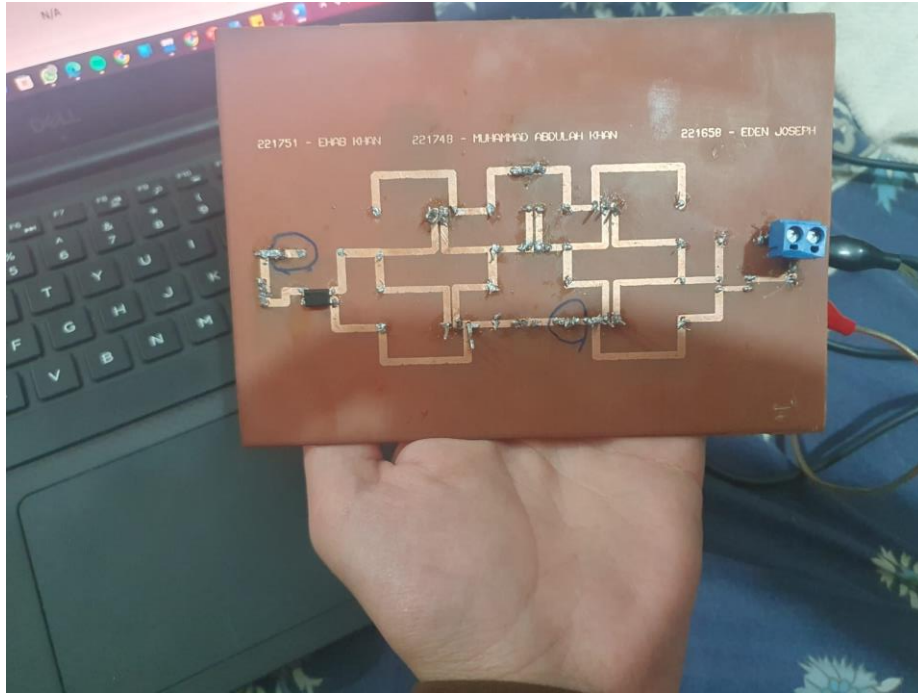

### 4.3 Finalization

The PCB Is In Perfect Working Condition Both On Simulation And Practical but due to a bit of a technical/design issue, we had to place a T-Block and PC817 optoisolater on the bottom copper side of the PCB circuit But it works fine and we are using T-Blocks as switches instead of buttons.

## 4.4 Bench Test Activity

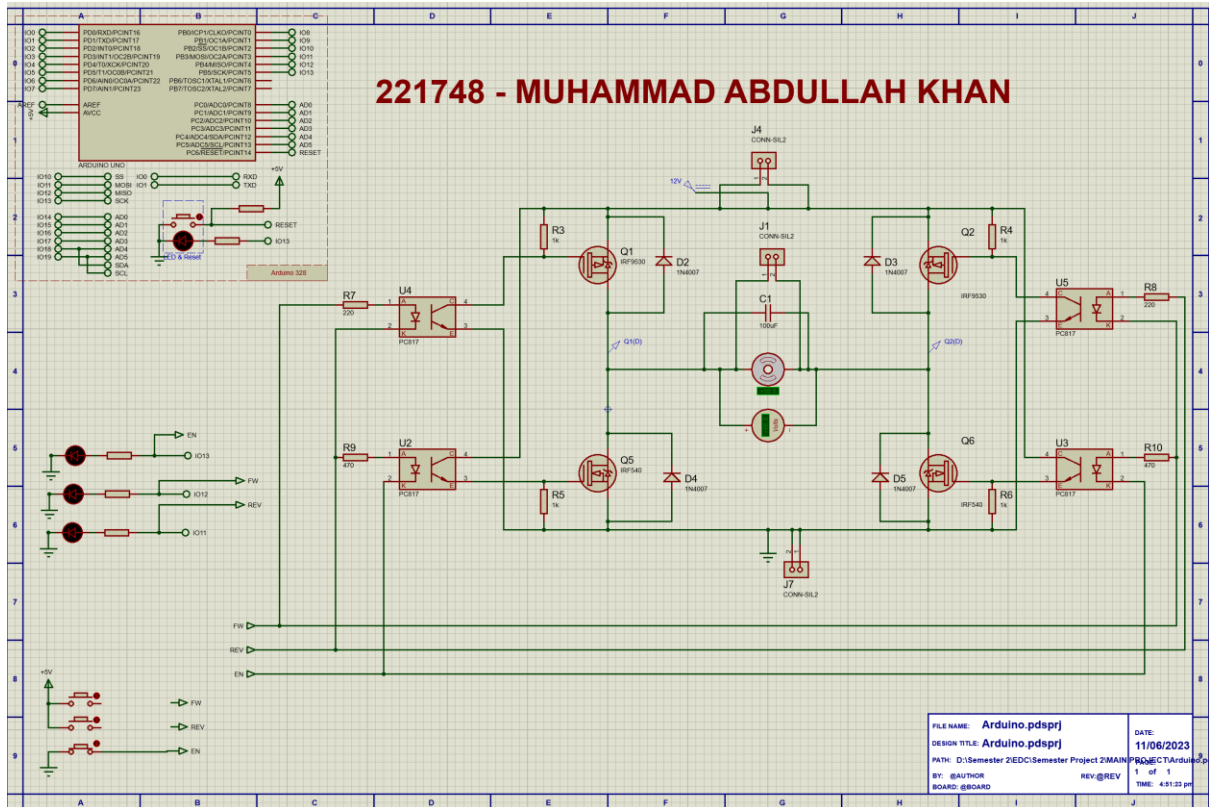

## 5 CONCLUSION

---

### 5.1 Summary:

To Summarize, we created an H-Bridge That will control direction of motors and other micro controlling devices using mosfets, flyback diodes and optocouplers which were the requirements.

### 5.2 Conclusion:

To Conclude, as far the project is concerned it has been a success and was executed to success and we are looking forward to further projects.

**THANK YOU !**